

EE - 2009

EE25BTECH11036 - M Chanakya Srinivas

1) The pressure coil of a dynamometer type wattmeter is

(GATE EE 2009)

- a) highly inductive
- b) highly resistive
- c) purely resistive
- d) purely inductive

2) The measurement system shown in the figure uses three sub-systems in cascade whose gains are specified as G_1 , G_2 and $\frac{1}{G_3}$. The relative small errors associated with each respective subsystem G_1 , G_2 , and G_3 are ε_1 , ε_2 , and ε_3 . The error associated with the output is: (GATE EE 2009)

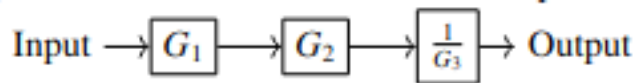


Fig. 1

- a) $\varepsilon_1 + \varepsilon_2 + \frac{1}{\varepsilon_3}$
- b) $\frac{\varepsilon_1 \cdot \varepsilon_2}{\varepsilon_3}$
- c) $\varepsilon_1 + \varepsilon_2 - \varepsilon_3$
- d) $\varepsilon_1 + \varepsilon_2 + \varepsilon_3$

3) The following circuit has a source voltage V_s as shown in the graph. The current through the circuit is also shown. (GATE EE 2009)



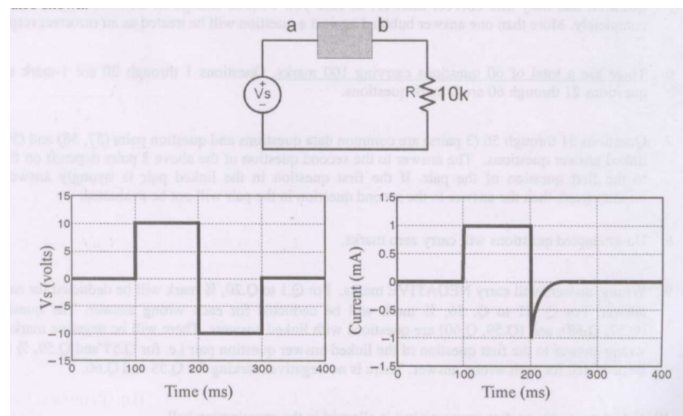


Fig. 2: *

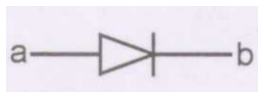
The elements connected between **a** and **b** could be




a)

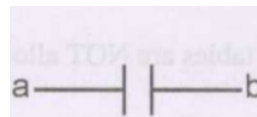

b)

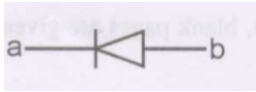

c)

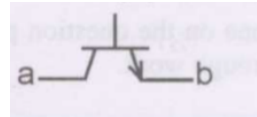

d)

- 4) The two inputs of a CRO are fed with two stationary periodic signals. In the X-Y mode, the screen shows a figure which changes from ellipse to circle and back to ellipse with its major axis changing orientation slowly and repeatedly. The following inference can be made from this. (GATE EE 2009)
- The signals are not sinusoidal
 - The amplitudes of the signals are very close but not equal
 - The signals are sinusoidal with their frequencies very close but not equal
 - There is a constant but small phase difference between the signals
- 5) The increasing order of speed of data access for the following devices is
 (i) Cache Memory (ii) CDROM (iii) Dynamic RAM (iv) Processor Registers (v) Magnetic Tape (GATE EE 2009)
- (v), (ii), (iii), (iv), (i)
 - (v), (ii), (iii), (i), (iv)
 - (ii), (i), (iii), (iv), (v)
 - (v), (ii), (i), (iii), (iv)
- 6) A field excitation of 20A in a certain alternator results in an armature current of 400A in short circuit and a terminal voltage of 2000 V on open circuit. The magnitude of the internal voltage drop within the machine at a load current of 200 A is (GATE EE 2009)
- 1 V
 - 10 V
 - 100 V
 - 1000 V
- 7) The current through the $2k\Omega$ resistance in the circuit shown is (GATE EE 2009)

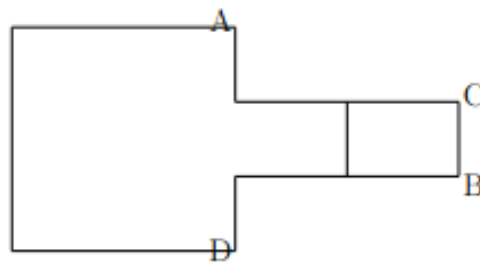


Fig. 3

- 0 mA
 - 1 mA
 - 2 mA
 - 6 mA
- 8) Out of the following plant categories (i) Nuclear (ii) Run-of-river (iii) Pump Storage (iv) Diesel the base load power plants are (GATE EE 2009)
- (i) and (ii)
 - (ii) and (iii)
 - (i), (ii) and (iii)

- d) (i), (iii) and (iv)
- 9) For a fixed value of complex power flow in a transmission line having a sending end voltage V , the real power loss will be proportional to (GATE EE 2009)
- V
 - V^2
 - $1/V^2$
 - $1/V$
- 10) How many 200W/220V incandescent lamps connected in series would consume the same total power as a single 100W/220V incandescent lamp? (GATE EE 2009)
- not possible
 - 4
 - 3
 - 2
- 11) A Linear Time Invariant system with an impulse response $h(t)$ produces output $y(t)$ when input $x(t)$ is applied. When the input $x(t - \tau)$ is applied to a system with impulse response $h(t - \tau)$, the output will be (GATE EE 2009)
- $y(t)$
 - $y(2(1 - t))$
 - $y(t - \tau)$
 - $y(t - 2\tau)$
- 12) The nature of feedback in the opamp circuit shown is (GATE EE 2009)

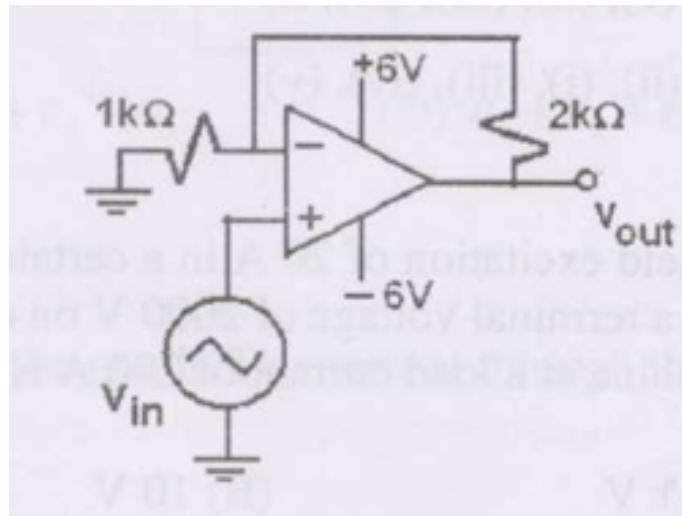


Fig. 4

- Current - Current feedback
 - Voltage - Voltage feedback
 - Current - Voltage feedback
 - Voltage - Current feedback
- 13) The complete set of only those Logic Gates designated as Universal Gates is (GATE EE 2009)
- NOT, OR and AND Gates
 - XNOR, NOR and NAND Gates
 - NOR and NAND Gates
 - XOR, NOR and NAND Gates

- 14) The single phase, 50Hz, iron core transformer in the circuit has both the vertical arms of cross sectional area 20 cm^2 and both the horizontal arms of cross sectional area 10 cm^2 . If the two windings shown were wound instead on opposite horizontal arms, the mutual inductance will (GATE EE 2009)

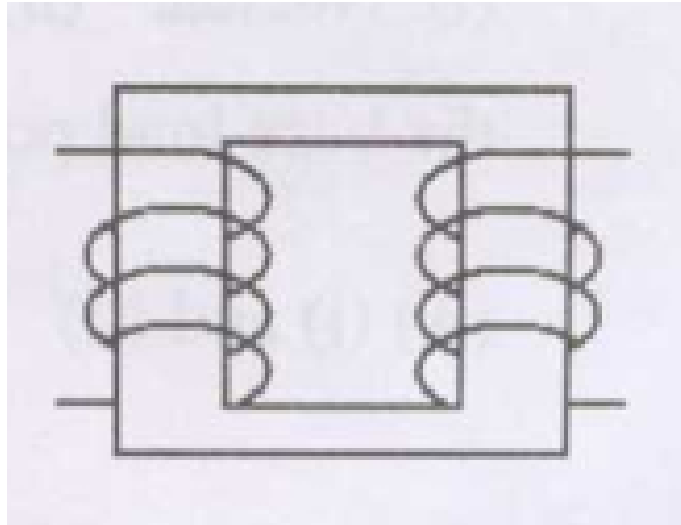


Fig. 5

- a) double
b) remain same
c) be halved
d) become one quarter
- 15) A 3-phase squirrel cage induction motor supplied from a balanced 3-phase source drives a mechanical load. The torque-speed characteristics of the motor (solid curve) and of the load (dotted curve) are shown. Of the two equilibrium points A and B, which of the following options correctly describes the stability of A and B? (GATE EE 2009)

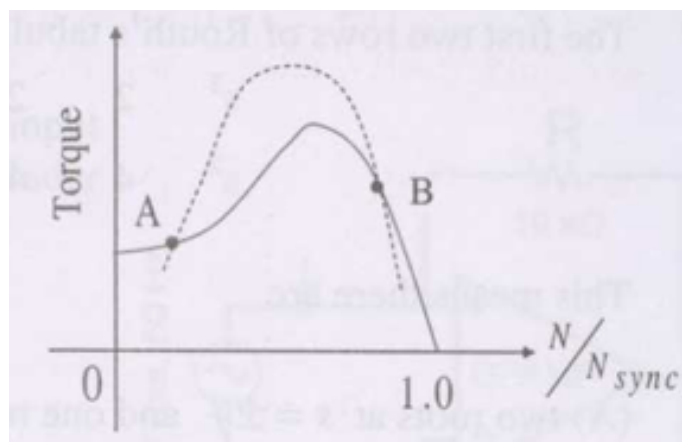


Fig. 6

- a) A is stable, B is unstable
b) A is unstable, B is stable
c) Both are stable
d) Both are unstable

- 16) An SCR is considered to be a semi-controlled device because (GATE EE 2009)
- it can be turned OFF but not ON with a gate pulse
 - it conducts only during one half-cycle of an alternating current wave
 - it can be turned ON but not OFF with a gate pulse
 - it can be turned ON only during one half-cycle of an alternating voltage wave
- 17) The polar plot of an open loop stable system is shown below. The closed loop system is (GATE EE 2009)

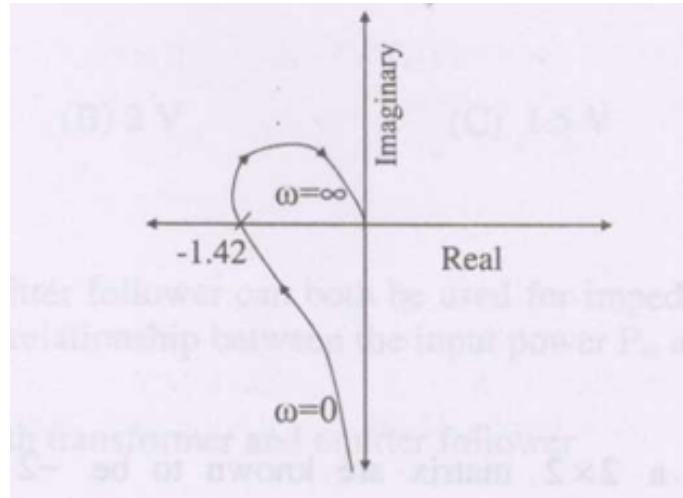


Fig. 7

- always stable
 - marginally stable
 - unstable with one pole on the right half s -plane
 - unstable with two poles on the right half s -plane
- 18) The first two rows of Routh's tabulation of a third order equation are as follows: (GATE EE 2009)

$$\begin{array}{ccc} s^3 & 2 & 2 \\ s^2 & 4 & 4 \end{array}$$

This means there are

- two roots at $s = \pm j$ and one root in right half s -plane
 - two roots at $s = \pm j2$ and one root in left half s -plane
 - two roots at $s = \pm j2$ and one root in right half s -plane
 - two roots at $s = \pm j$ and one root in left half s -plane
- 19) The asymptotic approximation of the log-magnitude vs frequency plot of a system containing only real poles and zeros is shown. Its transfer function is (GATE EE 2009)
- $\frac{10(s+5)}{s(s+2)(s+25)}$
 - $\frac{1000(s+5)}{s^2(s+2)(s+25)}$
 - $\frac{100(s+5)}{s(s+2)(s+25)}$
 - $\frac{80(s+5)}{s^2(s+2)(s+25)}$
- 20) The trace and determinant of a 2×2 matrix are known to be -2 and -35 respectively. Its eigenvalues are (GATE EE 2009)

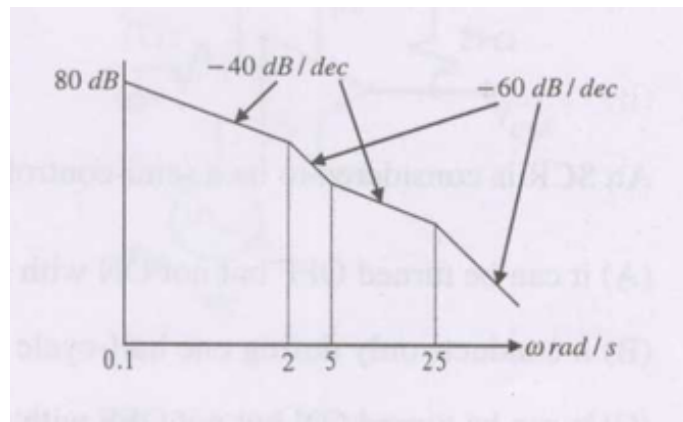


Fig. 8

- a) -30 and -5
- b) -37 and -1
- c) -7 and 5
- d) 17.5 and -2

21) The following circuit has $R = 10 \text{ k}\Omega$, $C = 10 \mu\text{F}$. The input voltage is a sinusoid at 50 Hz with an rms value of 10 V. Under ideal conditions, the current from the source is (GATE EE 2009)

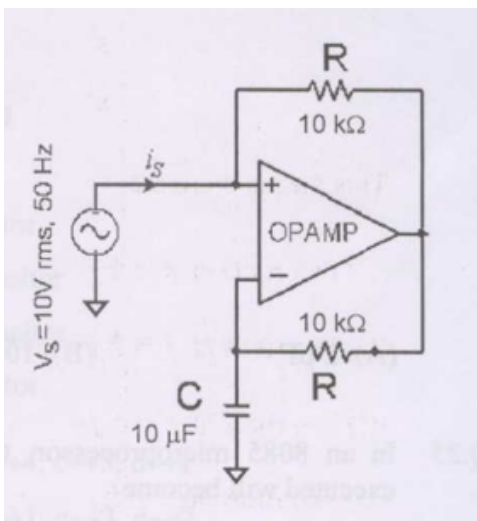


Fig. 9

- a) $10\pi \text{ mA}$ leading by 90°
- b) $20\pi \text{ mA}$ leading by 90°
- c) 10 mA leading by 90°
- d) $10\pi \text{ mA}$ lagging by 90°

22) In the figure shown, all elements used are ideal. For time $t < 0$, S_1 remained closed and S_2 open. At $t = 0$, S_1 is opened and S_2 is closed. If the voltage V_{C2} across the capacitor C_2 at $t = 0^-$ is 3 V, the voltage across the capacitor combination at $t = 0^+$ will be (GATE EE 2009)

- a) 1 V
- b) 2 V
- c) 1.5 V
- d) 3 V

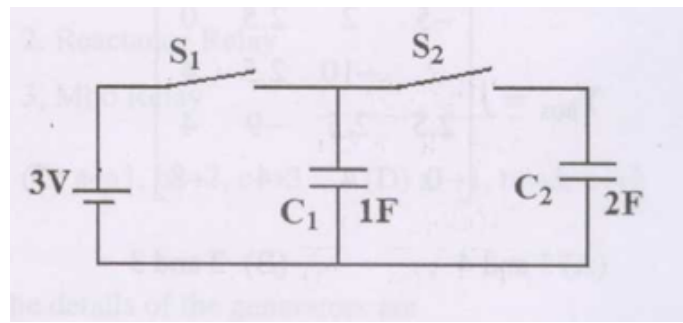


Fig. 10

- 23) Transformer and emitter follower can both be used for impedance matching at the output of an audio amplifier. The basic relationship between the input power P_{in} and output power P_{out} in both the cases is (GATE EE 2009)
- $P_{in} = P_{out}$ for both transformer and emitter follower
 - $P_{in} > P_{out}$ for both transformer and emitter follower
 - $P_{in} < P_{out}$ for transformer and $P_{in} = P_{out}$ for emitter follower
 - $P_{in} = P_{out}$ for transformer and $P_{in} < P_{out}$ for emitter follower
- 24) The equivalent capacitance of the input loop of the circuit shown is (GATE EE 2009)

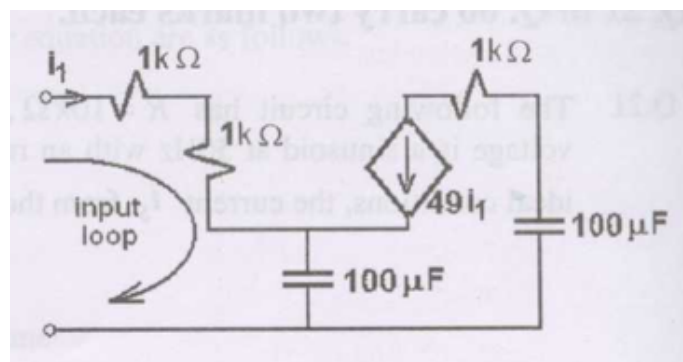


Fig. 11

- $2 \mu F$
 - $100 \mu F$
 - $200 \mu F$
 - $4 \mu F$
- 25) In an 8085 microprocessor, the contents of the Accumulator, after the following instructions are executed, will become (GATE EE 2009)
- XRA A
 MOV B, F0H
 SUB B
- 01H
 - 0FH
 - F0H
 - 10H
- 26) For the Y-bus matrix of a 4-bus system given in per unit, the buses having shunt elements are

$$(GATE EE 2009) Y_{BUS} = j \begin{pmatrix} -5 & 2 & 2.5 & 0 \\ 2 & -10 & 2.5 & 4 \\ 2.5 & 2.5 & -9 & 4 \\ 0 & 4 & 4 & -8 \end{pmatrix}$$

- a) 3 and 4
- b) 2 and 3
- c) 1 and 2
- d) 1, 2 and 4

27) The unit-step response of a unity feedback system with open loop transfer function

$$G(s) = \frac{K}{(s+1)(s+2)}$$

is shown in the figure. The value of K is

(GATE EE 2009)

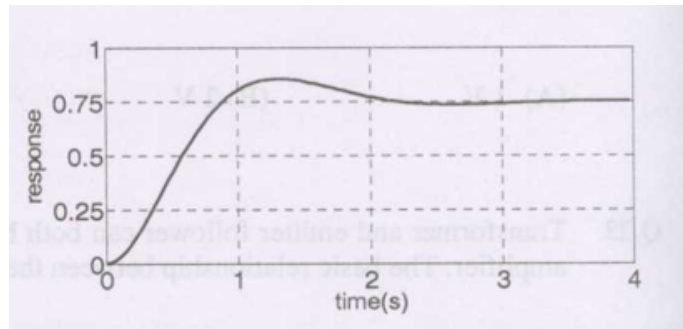


Fig. 12

- a) 0.5
- b) 2
- c) 4
- d) 6

28) The open loop transfer function of a unity feedback system is given by

$$G(s) = \frac{e^{-0.1s}}{s}$$

The gain margin of this system is

(GATE EE 2009)

- a) 11.95 dB
- b) 17.67 dB
- c) 21.33 dB
- d) 23.9 dB

29) Match the items in List-I with the items in List-II and select the correct answer using the codes

List I

List II

given below the lists. (GATE EE 2009)

- a. improve power factor
- b. reduce the current ripples
- c. increase the power flow in line
- d. reduce the Ferranti effect

- 1. shunt reactor
- 2. shunt capacitor
- 3. series capacitor
- 4. series reactor

- a) a - 2, b - 3, c - 4, d - 1
- b) a - 2, b - 4, c - 3, d - 1
- c) a - 4, b - 3, c - 1, d - 2

d) a - 4, b - 1, c - 3, d - 2

30) Match the items in List-I with the items in List-II and select the correct answer using the codes

	List I	List II
given below the lists.	a. Short Line	1. Ohm Relay
(GATE EE 2009)	b. Medium Line	2. Reactance Relay
	c. Long Line	3. Mho Relay

a) a - 2, b - 1, c - 3

b) a - 3, b - 2, c - 1

c) a - 1, b - 2, c - 3

d) a - 1, b - 3, c - 2

31) Three generators are feeding a load of 100 MW. The details of the generators are: (GATE EE

	Rating (MW)	Efficiency (%)	Regulation (p.u.) on 100 MVA base
2009) Generator-1	100	100	20
Generator-2	100	100	30
Generator-3	100	100	40
			0.02
			0.04
			0.03

In the event of increased load power demand, which of the following will happen? (GATE EE 2009)

a) All the generators will share equal power

b) Generator-3 will share more power compared to Generator-1

c) Generator-1 will share more power compared to Generator-2

d) Generator-2 will share more power compared to Generator-3

32) A 500 MW, 21 kV, 50 Hz, 3-phase, 2-pole synchronous generator having a rated power factor = 0.9, has a moment of inertia of $27.5 \times 10^3 \text{ kg-m}^2$. The inertia constant (H) will be (GATE EE 2009)

a) 2.44 s

b) 2.71 s

c) 4.88 s

d) 5.42 s

33) $f(x, y)$ is a continuous function defined over $(x, y) \in [0, 1] \times [0, 1]$. Given the two constraints, $x > y^2$ and $y > x^2$, the volume under $f(x, y)$ is (GATE EE 2009)

a) $\int_0^1 \int_{y^2}^1 f(x, y) dx dy$

b) $\int_0^1 \int_{x^2}^1 f(x, y) dy dx$

c) $\int_0^1 \int_0^{\sqrt{x}} f(x, y) dy dx$

d) $\int_0^1 \int_0^{\sqrt{y}} f(x, y) dx dy$

34) Assume for simplicity that N people, all born in April (a month of 30 days), are collected in a room. Consider the event of at least two people in the room being born on the same date of the month, even if in different years, e.g. 1980 and 1985. What is the smallest N so that the probability of this event exceeds 0.5? (GATE EE 2009)

a) 20

b) 7

c) 15

d) 16

35) A cascade of 3 Linear Time Invariant systems is causal and unstable. From this, we conclude that (GATE EE 2009)

a) Each system in the cascade is individually causal and unstable

- b) At least one system is unstable and at least one system is causal
- c) At least one system is causal and all systems are unstable
- d) The majority are unstable and the majority are causal

36) The Fourier Series coefficients, of a periodic signal $x(t)$, expressed as

$$x(t) = \sum_{k=-\infty}^{\infty} a_k e^{j2\pi kt/T}$$

are given by:

(GATE EE 2009)

$$a_{-2} = 2 - j1, \quad a_{-1} = 0.5 + j0.2, \quad a_0 = j2, \quad a_1 = 0.5 - j0.2, \quad a_2 = 2 + j1, \quad a_k = 0 \quad \text{for } |k| > 2.$$

Which of the following is true?

(GATE EE 2009)

- a) $x(t)$ has finite energy because only finitely many coefficients are non-zero
- b) $x(t)$ has zero average value because it is periodic
- c) The imaginary part of $x(t)$ is constant
- d) The real part of $x(t)$ is even

37) The z-transform of a signal $x[n]$ is given by

$$4z^3 + 3z^{-1} + 2 - 6z^2 + 2z^3.$$

It is applied to a system with a transfer function

$$H(z) = 3z^{-1} - 2.$$

Let the output be $y(n)$. Which of the following is true?

(GATE EE 2009)

- a) $y(n)$ is non causal with finite support
- b) $y(n)$ is causal with infinite support
- c) $y(n) = 0$ for $|n| > 3$
- d) $\text{Re}[Y(z)]_{z=e^{j\theta}} = -\text{Re}[Y(z)]_{z=e^{-j\theta}}, \quad \text{Im}[Y(z)]_{z=e^{j\theta}} = \text{Im}[Y(z)]_{z=e^{-j\theta}}, \quad -\pi \leq \theta < \pi$

38) A cubic polynomial with real coefficients

(GATE EE 2009)

- a) can possibly have no extrema and no zero crossings
- b) may have up to three extrema and up to two zero crossings
- c) cannot have more than two extrema and more than three zero crossings
- d) will always have an equal number of extrema and zero crossings

39) Let

$$(x^2 - 117 = 0)$$

. The iterative steps for the solution using Newton-Raphson's method is given by (GATE EE 2009)

a)

$$(x_{k+1} = \frac{1}{2} \left(x_k + \frac{117}{x_k} \right))$$

b)

$$(x_{k+1} = x_k - \frac{117}{x_k})$$

c)

$$(x_{k+1} = x_k - \frac{x_k}{117})$$

d)

$$(x_{k+1} = x_k - \frac{1}{2} \left(x_k + \frac{117}{x_k} \right))$$


40)

$$\mathbf{F}(x, y) = (x^2 + xy)\hat{a}_x + (y^2 + xy)\hat{a}_y.$$


Its line integral over the straight line from $(x, y) = (0, 2)$ to $(2, 0)$ evaluates to: (GATE EE 2009)

- a) -8
- b) 4
- c) 8
- d) 0

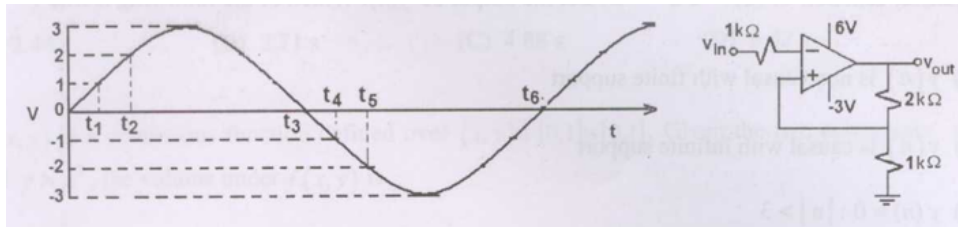
- 41) An ideal opamp circuit and its input waveform are shown in the figures. The output waveform of this circuit will be: (GATE EE 2009)




- a) (Waveform A)

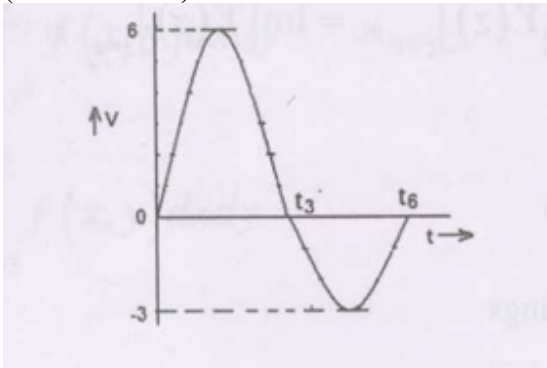


- b) (Waveform B)

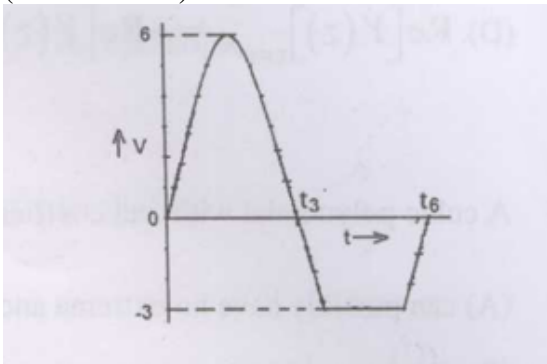

- c) (Waveform C)

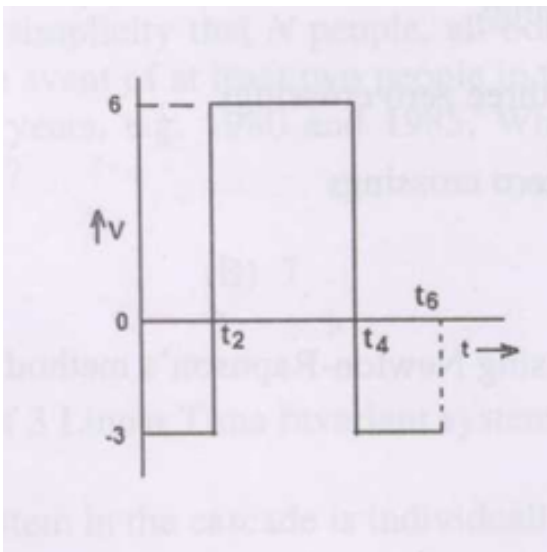


d) (Waveform D)

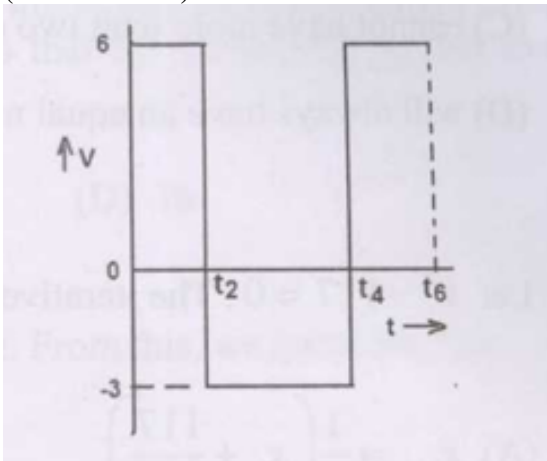

- 42) A 220 V, 50 Hz, single-phase induction motor has the following connection diagram and winding orientations shown. MM' is the axis of the main stator winding (M_1M_2), and AA' is that of the auxiliary winding (A_1A_2). Directions of the winding axes indicate direction of flux when currents in the windings are in the directions shown. Parameters of each winding are indicated. When switch S is closed, the motor:

(GATE EE 2009)

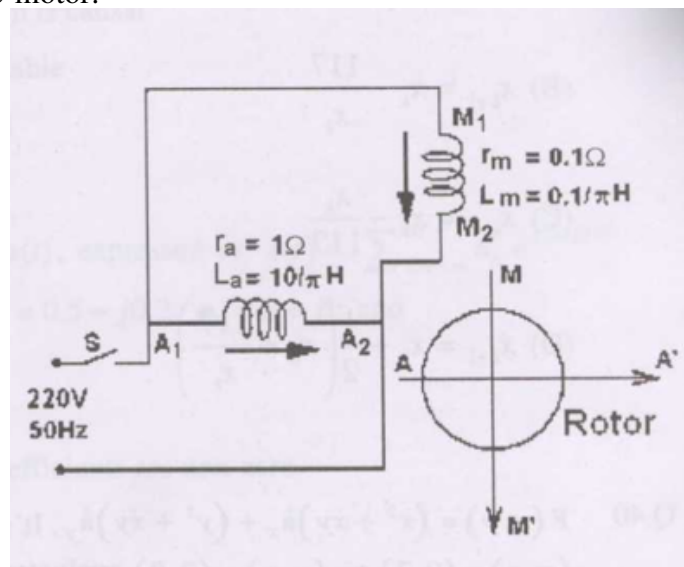

- a) rotates clockwise

- b) rotates anticlockwise
 c) does not rotate
 d) rotates momentarily and comes to a halt
- 43) The circuit shows an ideal diode connected to a pure inductor and driven by a purely sinusoidal 50 Hz voltage source. The voltage source is

$$v_s = 10 \sin(100\pi t).$$



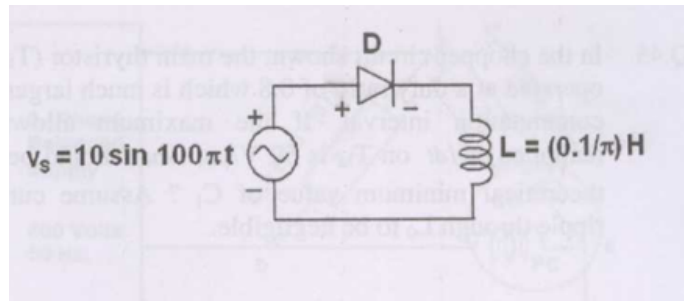


Fig. 13

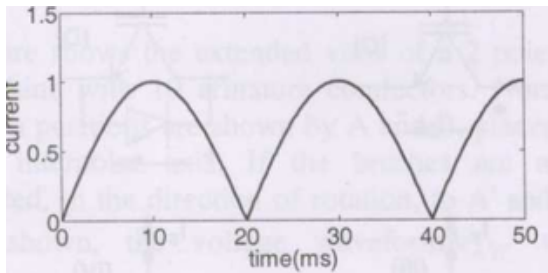
Under ideal conditions, the current waveform through the inductor will look like: (GATE EE 2009)




a)

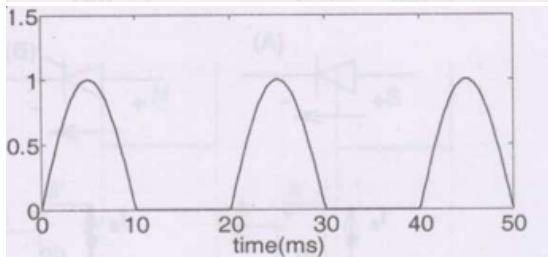

b)

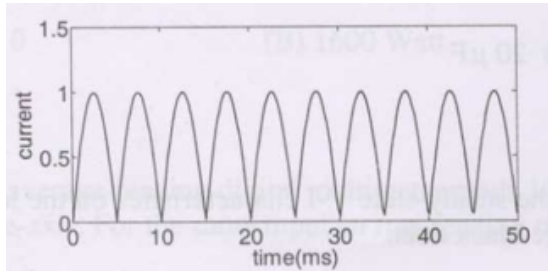

c)

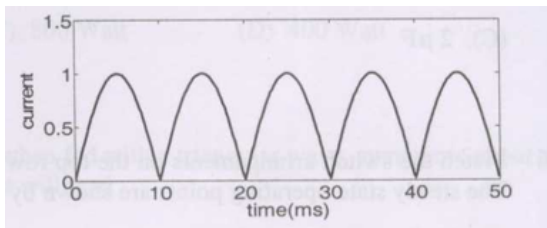

d)

- 44) The current source inverter shown in the figure is operated by alternately turning on thyristor pairs (T1, T2) and (T3, T4). If the load is purely resistive, the theoretical maximum output frequency obtainable will be:

(GATE EE 2009)


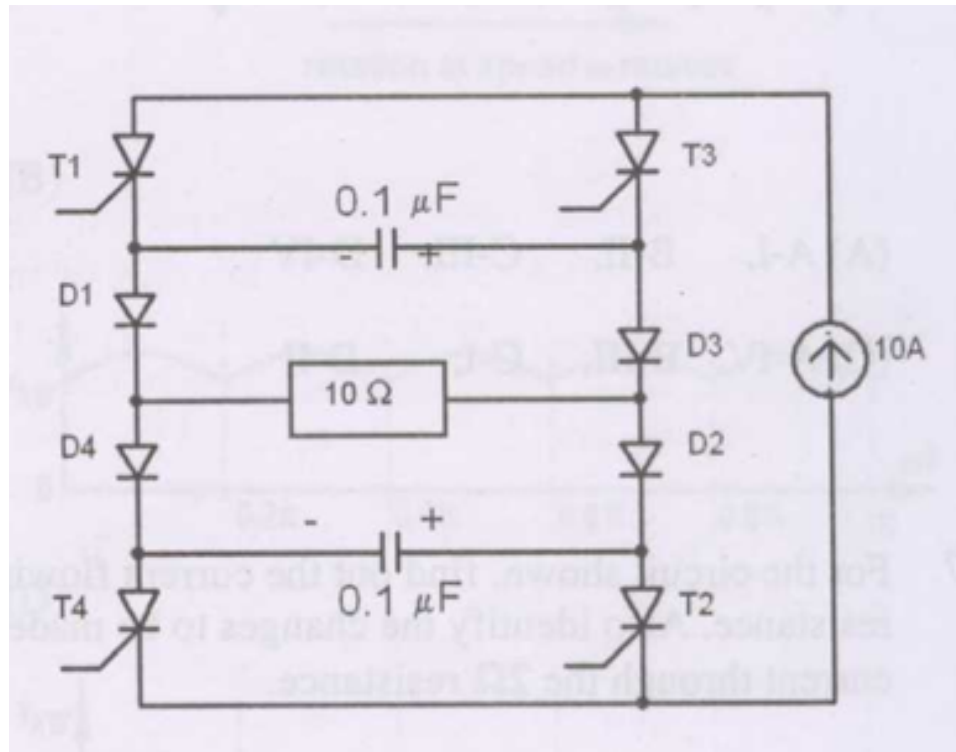


Fig. 14

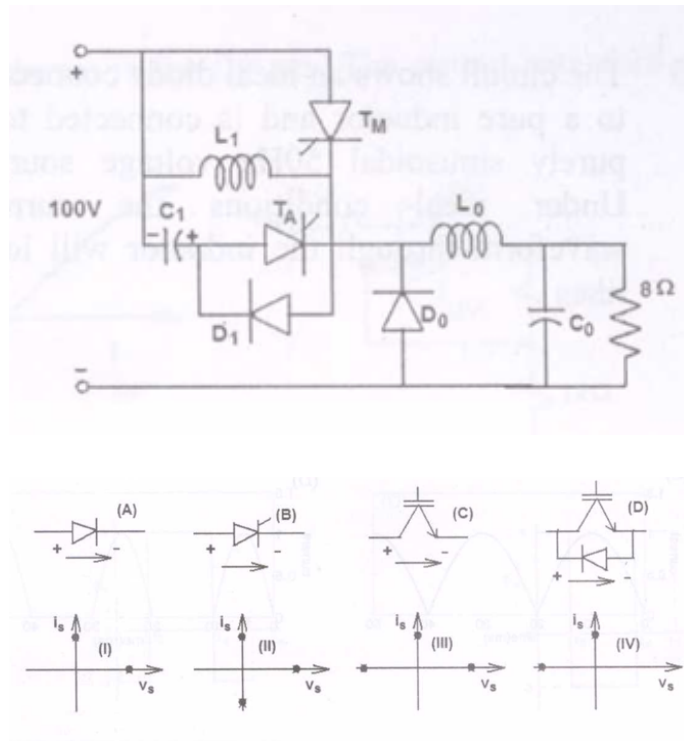- a) 125 kHz
 b) 250 kHz
 c) 500 kHz
 d) 50 kHz
- 45) In the chopper circuit shown, the main thyristor (T_M) is operated at a duty ratio of 0.8 which is much larger than the commutation interval. If the maximum allowable reapplied dv/dt on T_M is $50 \text{ V}/\mu\text{s}$, what should be the theoretical minimum value of C_1 ? Assume current ripple through L_0 to be negligible. (GATE EE 2009)
- a) $0.2 \mu\text{F}$
 b) $0.02 \mu\text{F}$
 c) $2 \mu\text{F}$
 d) $20 \mu\text{F}$
- 46) Match the switch arrangements on the top row to the steady-state V-I characteristics on the lower row. The steady-state operating points are shown by large black dots. (GATE EE 2009)
- a) A-I, B-II, C-III, D-IV



- b) A-II, B-IV, C-I, D-III
- c) A-IV, B-III, C-I, D-II
- d) A-IV, B-III, C-II, D-I

47) For the circuit shown, find out the current flowing through the 2Ω resistance. Also, identify the changes to be made to double the current flow through the 2Ω resistance. (GATE EE 2009)

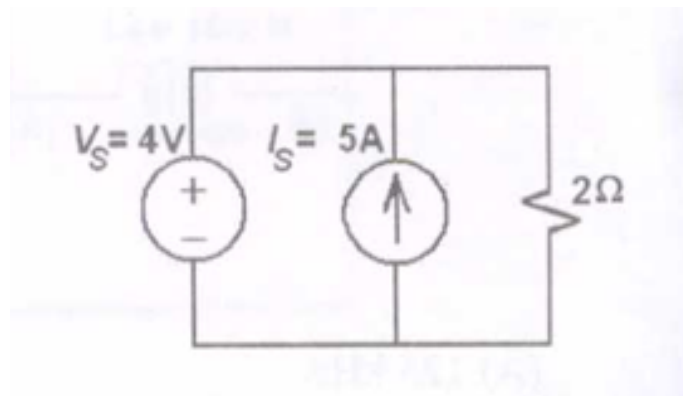


Fig. 15: *

- a) (5A; Put $V_s = 20V$)
- b) (2A; Put $V_s = 8V$)
- c) (5A; Put $I_s = 10A$)
- d) (7A; Put $I_s = 12A$)

48) The figure shows a three-phase delta connected load supplied from a 400 V, 50 Hz, 3-phase balanced source. The pressure coil (PC) and current coil (CC) of a wattmeter are connected to the load as shown, with the coil polarities suitably selected to ensure a positive deflection.

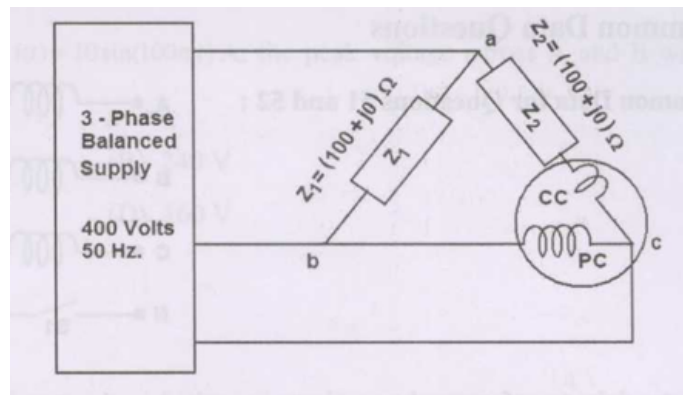
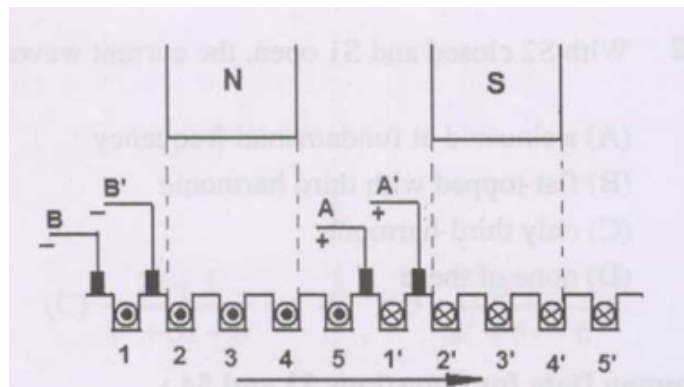
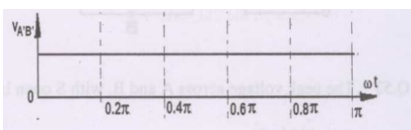


Fig. 16: *


The wattmeter reading will be:

(GATE EE 2009)

- a) 0
 - b) 1600 W
 - c) 800 W
 - d) 400 W
- 49) An average-reading digital multimeter reads 10 V when fed with a triangular wave, symmetric about the time-axis. For the same input, an rms-reading meter will read: (GATE EE 2009)
- a) $\frac{20}{\sqrt{3}}$
 - b) $\frac{10}{\sqrt{3}}$
 - c) $20\sqrt{3}$
 - d) $10\sqrt{3}$
- 50) The figure shows the extended view of a 2-pole DC machine with 10 armature conductors. Normal brush positions are shown by A and B, placed at the interpolar axis. If the brushes are now shifted, in the direction of rotation, to A' and B' as shown, the voltage waveform $V_{A'B'}$ will resemble: (GATE EE 2009)

Fig. 17: rotation speed at ω rad/sec


a)

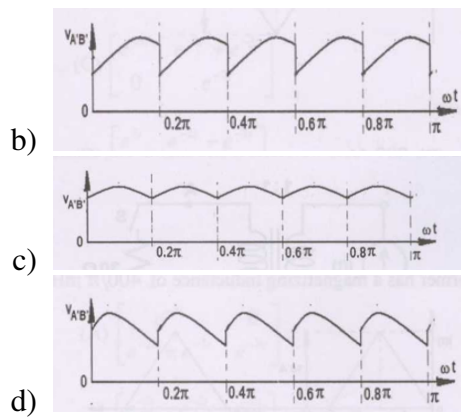

Common Data Questions

Common Data for Questions 51 and 52:

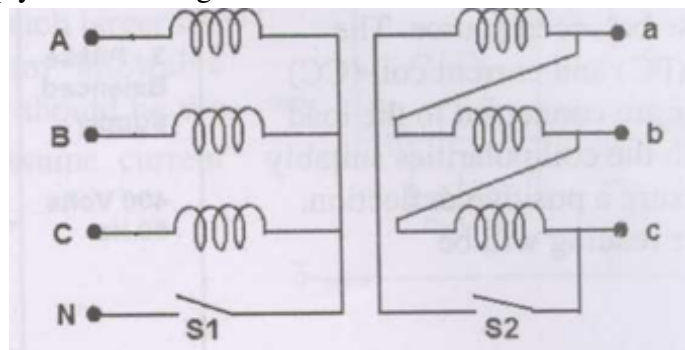
The star-delta transformer shown below is excited on the star side with a balanced, 4-wire, 3-phase, sinusoidal voltage supply of rated magnitude. The transformer is under no load condition.



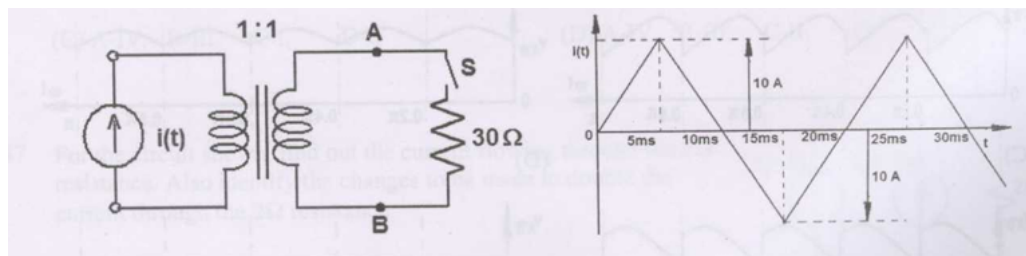- 51) With both S_1 and S_2 open, the core flux waveform will be: (GATE EE 2009)
- a sinusoid at fundamental frequency
 - flat-topped with third harmonic
 - peaky with third-harmonic
 - none of these
- 52) With S_2 closed and S_1 open, the current waveform in the delta winding will be: (GATE EE 2009)
- a sinusoid at fundamental frequency
 - flat-topped with third harmonic
 - only third-harmonic
 - none of these

Common Data for Questions 53 and 54:

The circuit diagram shows a two-winding, lossless transformer with no leakage flux, excited from a current source $i(t)$ whose waveform is also shown. The transformer has a magnetizing inductance of $\frac{400}{\pi}$ mH.



- 53) The peak voltage across A and B, with S open, is: (GATE EE 2009)

- a) $\frac{400}{\pi}$ V
- b) 800 V
- c) $\frac{4000}{\pi}$ V
- d) $\frac{800}{\pi}$ V

54) If the waveform of $i(t)$ is changed to

$$i(t) = 10 \sin(100\pi t) \text{ A,}$$

the peak voltage across A and B with S closed is:

(GATE EE 2009)

- a) 400 V
- b) 240 V
- c) 320 V
- d) 160 V

Common Data for Questions 55 and 56

A system is described by the following state and output equations:

$$\frac{dx_1(t)}{dt} = -3x_1(t) + x_2(t) + 2u(t) \quad \frac{dx_2(t)}{dt} = -2x_2(t) + u(t) \quad y(t) = x_1(t)$$

where $u(t)$ is the input and $y(t)$ is the output.

55) The system transfer function is:

(GATE EE 2009)

- a) $\frac{s+2}{s^2+5s-6}$
- b) $\frac{s+3}{s^2+5s+6}$
- c) $\frac{s^2+5s+6}{2s+5}$
- d) $\frac{s^2+5s+6}{s^2+5s-6}$

56) The state-transition matrix of the above system is:

(GATE EE 2009)

a)

$$\begin{pmatrix} e^{-3t} & 0 \\ e^{-2t} + e^{-3t} & e^{-2t} \end{pmatrix}$$

b)

$$\begin{pmatrix} e^{-3t} & e^{-2t} - e^{-3t} \\ 0 & e^{-2t} \end{pmatrix}$$

c)

$$\begin{pmatrix} e^{-3t} & e^{-2t} + e^{-3t} \\ 0 & e^{-2t} \end{pmatrix}$$


d)

$$\begin{pmatrix} e^{-3t} & e^{-2t} - e^{-3t} \\ 0 & e^{-2t} \end{pmatrix}$$

Linked Answer Questions

Statement for Questions 57 and 58:

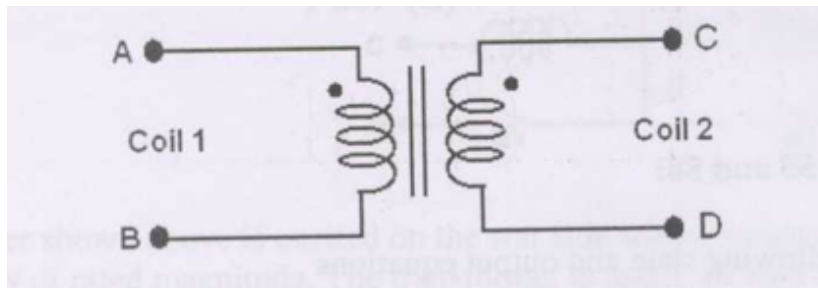The figure below shows coils 1 and 2, with dot markings as indicated, having 4000 and 6000 turns respectively. Both the coils have a rated current of 25 A. Coil 1 is excited with single-phase, 400 V, 50 Hz supply.




- 57) The coils are to be connected to obtain a single-phase, 400/1000 V, auto-transformer to drive a load of 10 kVA. Which of the options should be exercised to realize the required auto-transformer? (GATE EE 2009)
- Connect A and D; Common B
 - Connect B and D; Common C
 - Connect A and C; Common B
 - Connect A and C; Common D
- 58) In the autotransformer obtained in Question 57, the current in each coil is: (GATE EE 2009)
- Coil-1 is 25 A and Coil-2 is 10 A
 - Coil-1 is 10 A and Coil-2 is 25 A
 - Coil-1 is 10 A and Coil-2 is 15 A
 - Coil-1 is 15 A and Coil-2 is 10 A

Linked Answer Questions

Statement for Questions 59 and 60:

The circuit diagram is shown below:

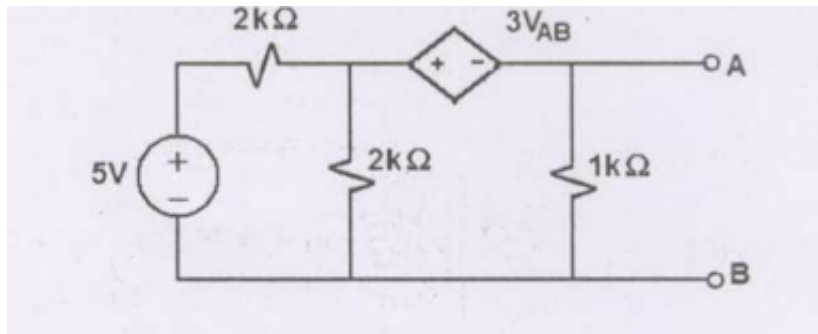

- 59) For the circuit given above, the Thevenin's resistance across the terminals A and B is: (GATE EE 2009)
- 0.5 k Ω
 - 0.2 k Ω
 - 1 k Ω
 - 0.11 k Ω
- For the circuit given above, the Thevenin's voltage across the terminals A and B is: (GATE EE 2009)
- 1.25 V
 - 0.25 V
 - 1 V
 - 0.5 V

— END OF THE QUESTION PAPER —